


Six Stage Pipelined Design Implementation

Design Report


Divycharaneeswar R P
170260018

Thoutam Shiva Teja
170260035

Instruction Fetch Stage

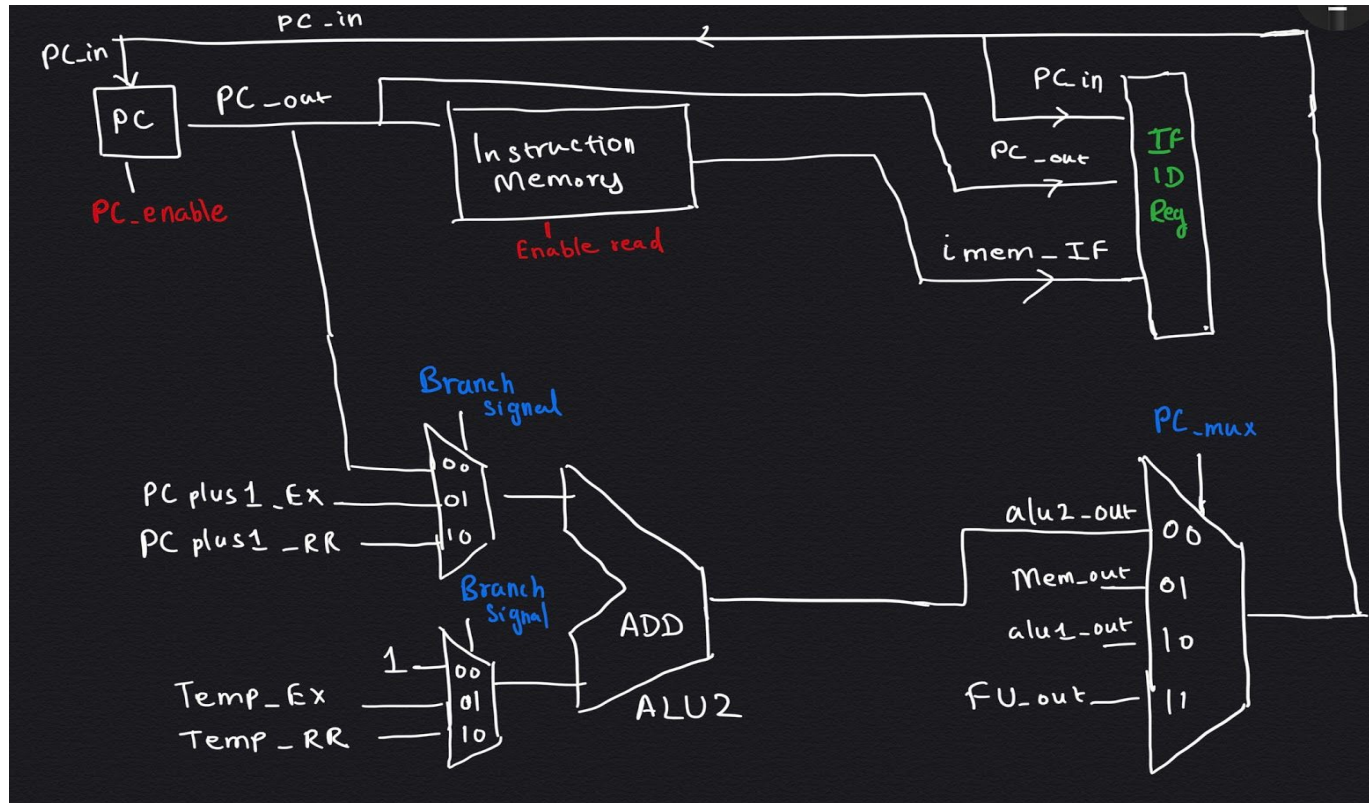


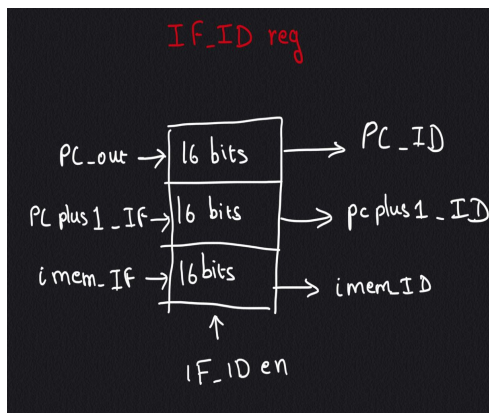1. **PC register:** Stores the PC value of the current instruction.
2. **Instruction memory :** Instruction Memory from which the instruction is obtained.
3. **ALU2 :** Used to update the PC value($PC+1$ / $PC+Imm$)
4. **Branch Signal**
 - a. 01 if BEQ , we get to know know in Execution stage
Temp_EX -- Immediate value to be added
 - b. 10 if JAL , we designed such that Imm is available from RR stage
Temp_RR -- Immediate value to be added
 - c. 00 else
5. **Enable read =1 always**
6. **PC_enable = 1 if no stalling in IF stage**
7. **PC_MUX** --Decides the PC value when the destination register is R7(Considered that on writing in R7 register also changes the PC)
 - a. 10 if ADD/ADI/NDU and If the destination register is R7
 - b. 01 if LW/LM and If the destination register is R7
 - c. 11 if LHI/JLR and If the destination register is R7
 - d. 00 else



- ❖ PCplus1_IF is connected with input of PC
 - ❖ imem_IF is connected with output of the instruction memory
 - ❖ IF_ID = 1 if no stalling in IF stage
-

Instruction Decoder

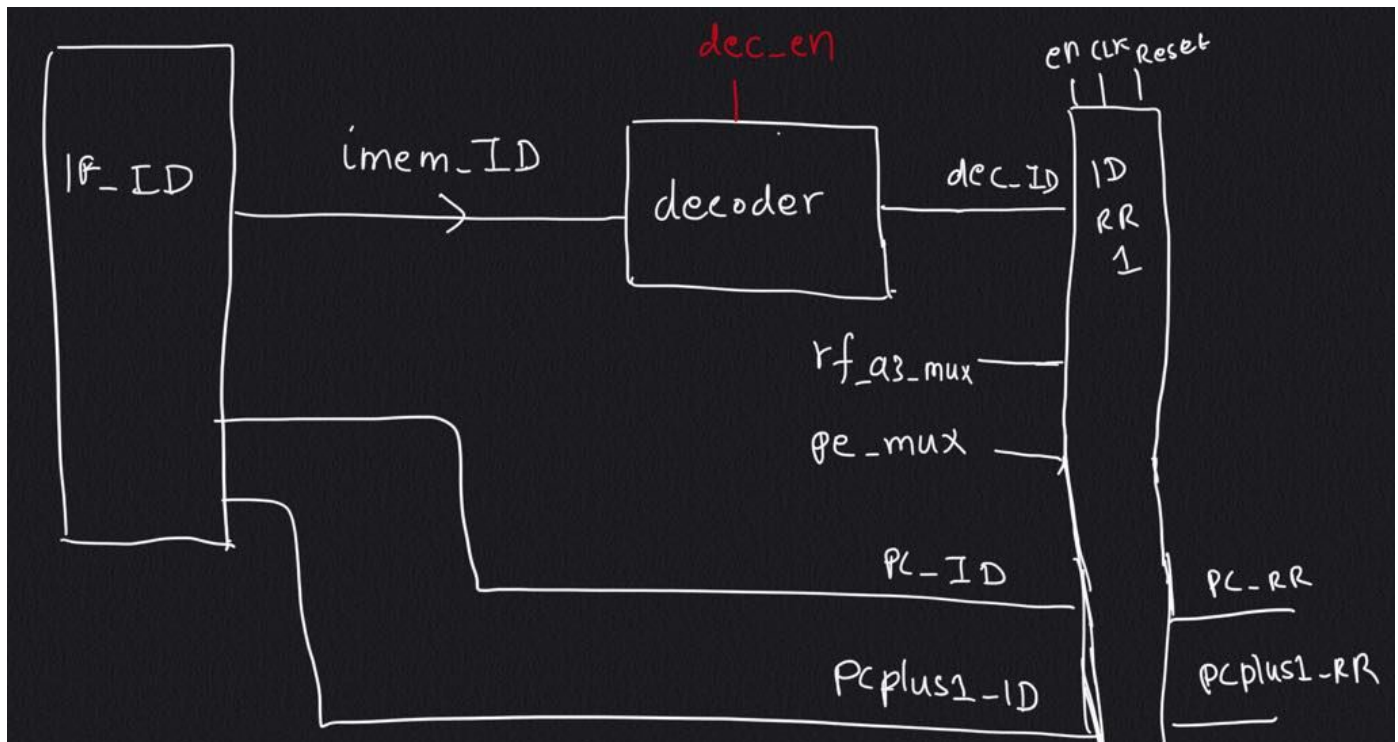


In ID stage, the instruction is passed to the decoder from the IF_ID register. Two pipeline registers ID_RR1 and ID_RR2 are used, where ID_RR1 takes care of the LM/SM instructions.

1. **Decoder :**


- Takes the input as the instruction and gives output in 45 bits which includes
- If **decoder_enable** is set, then **mem_wr_en**, **c flag_en**, **z flag_en** are set.

Inside ID_RR

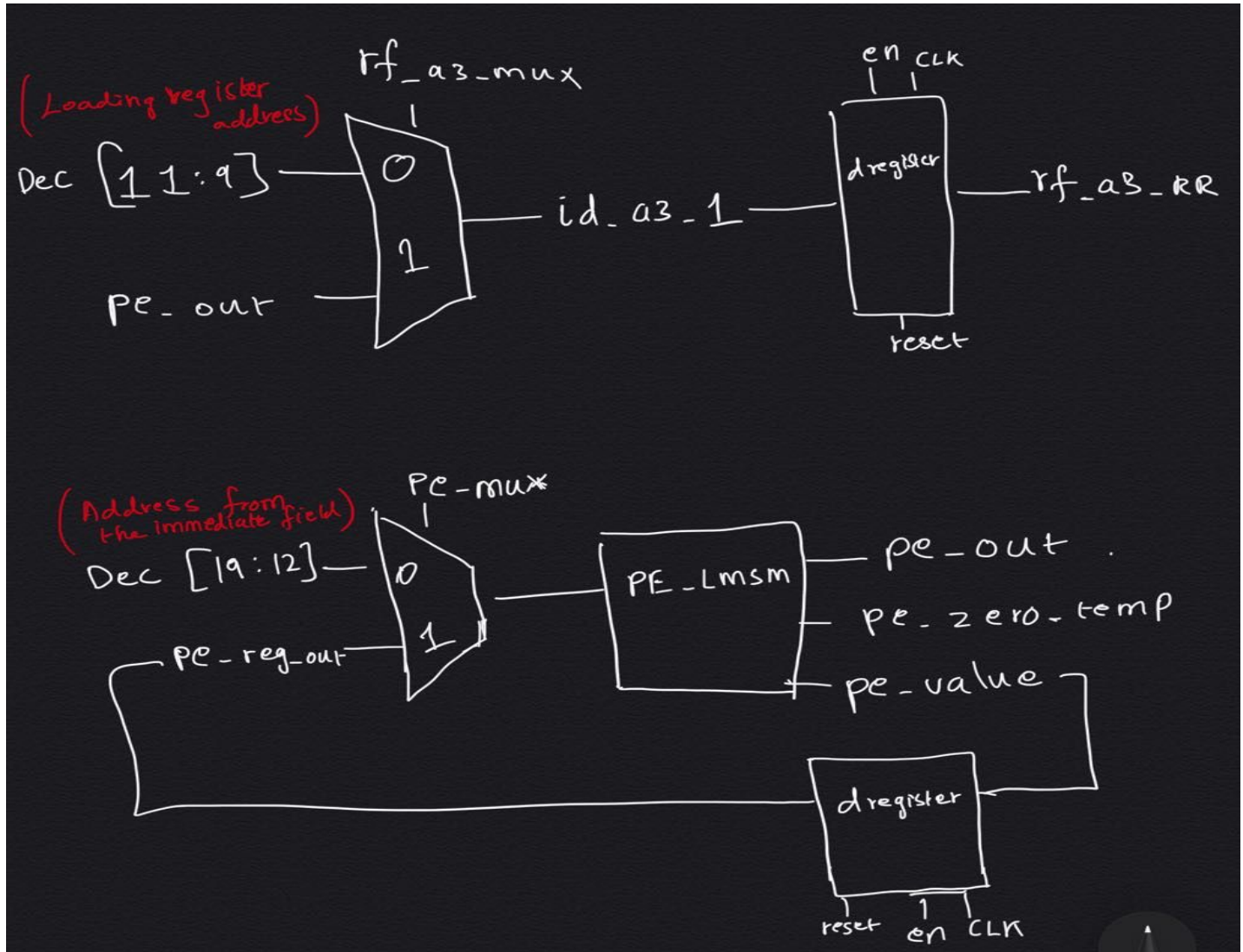


2. **Rf_a3_mux** : It is 1 when the instruction is LM and this mux gives the address of the register to loaded.
3. **PE_lmsm** :
 - a. This block takes the address from the immediate field and gives output as the address of the register(**pe_out**) to be used in LM / SM instruction.
 - b. It also updates the address from the immediate field of already used register with 0 (**pe_value**) and when all 8 bits are zero in the address, the **pc_zero** is set as 1.
4. **PE_mux** :
 - a. This chooses between the address from the immediate field or the updated address from the **PE_lmsm** block

Register Read

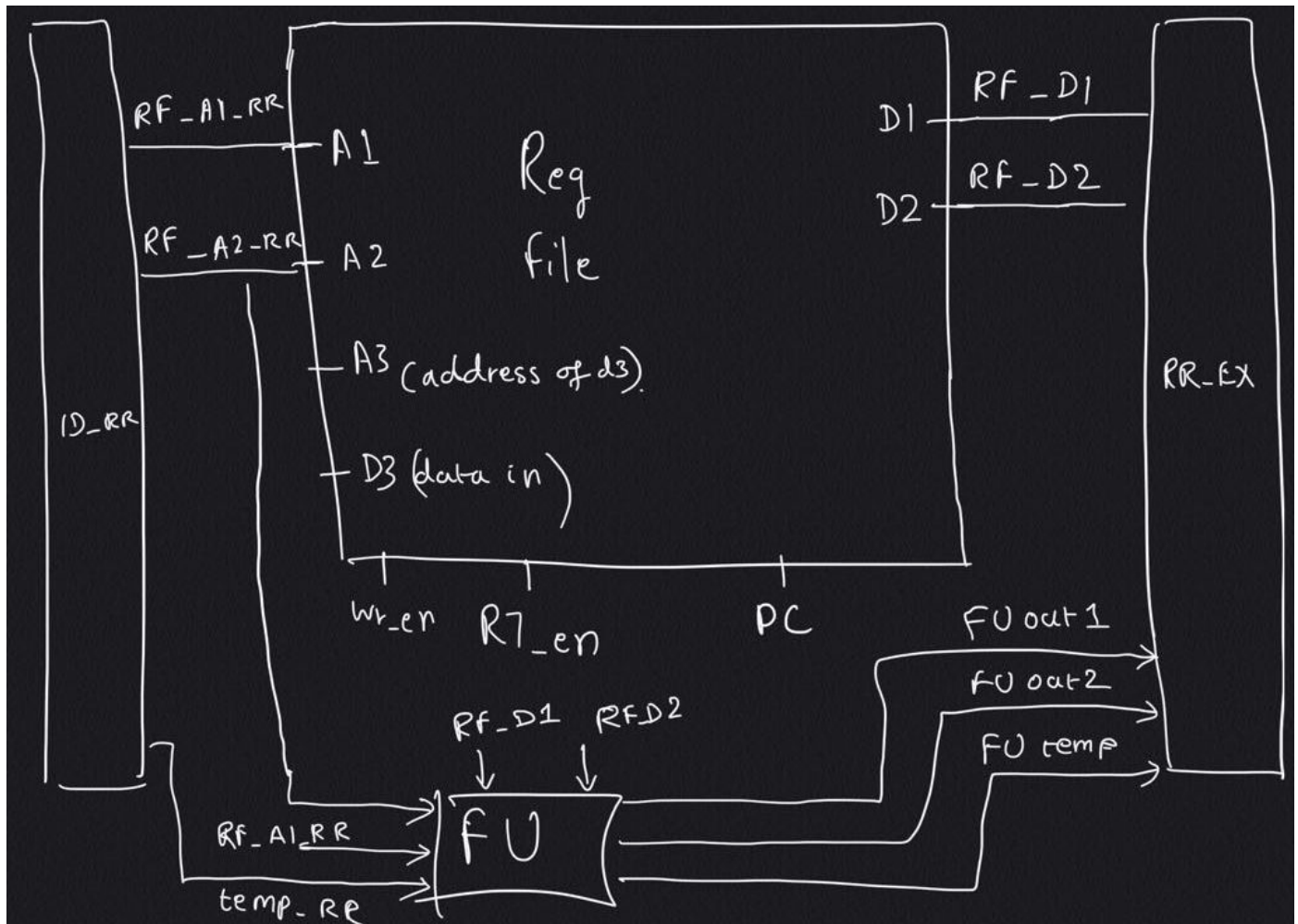



1. This stage has the forwarding unit and the register file
2. FU out1 goes for alu_in1
3. FU out2 goes for alu_in2
4. FU_temp is data in for memory

Execution

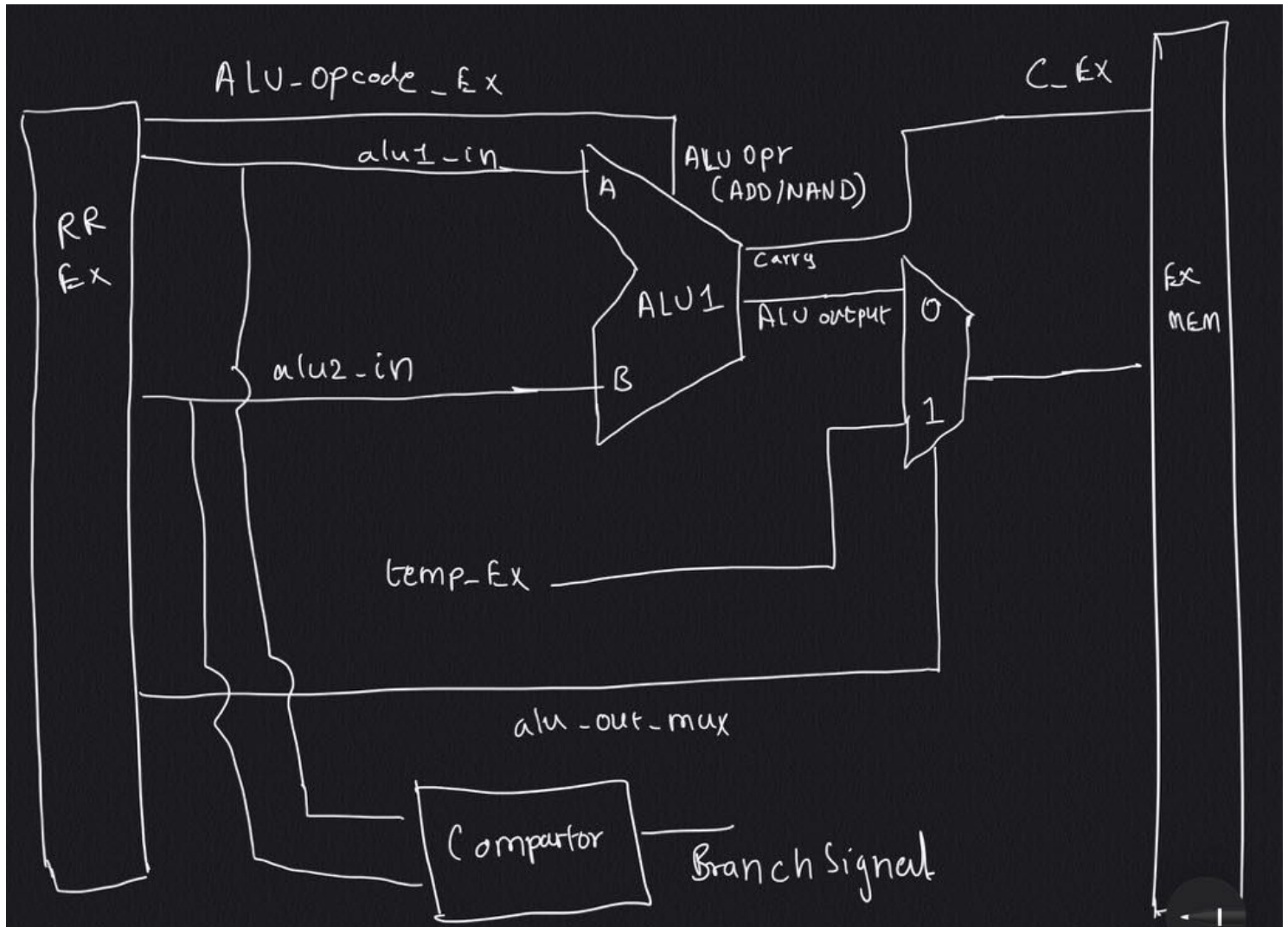


1. **ALU** : Perform ADD, NAND operation
2. **Comparator** : Checks the equality and generates branch signal for choosing the updated PC in IF stage
3. **Temp EX** : Has the sign extended value or the content of the register depending on the instruction
4. **ALU_out_mux**: decided from the 3rd bit of controlpoint

Memory Write/Read

  

1. **MEM** : Data memory from which the instruction read data or writes data.
2. **MEM wr en block**:
 - a. During the store instruction if the memory stage is needed to flushed then wr_en is made 0
 - b. In other cases the wr_en signal from the decoder is taken
3. The wr_en_update corresponds to the wr_en for ADC,ADZ,NDC,NDZ instructions

WriteBack

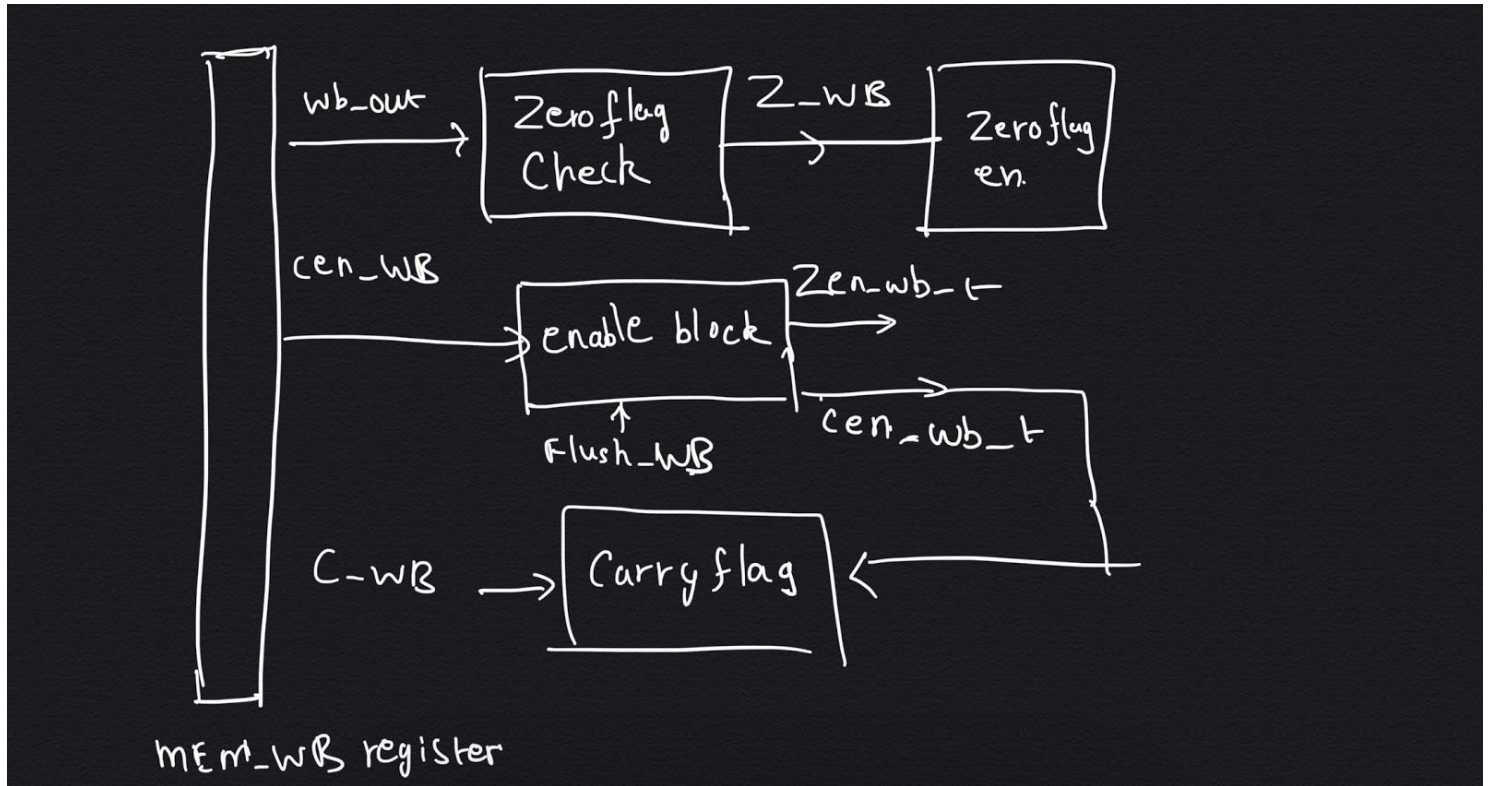

1. **Enable block**:
 - a. If flush is active for WB stage then it doesn't write enable the zero and carry flag.
 - b. If there is no flush then write enable signals for carry and zero flag received from decoder is taken .
2. **Zero flag check**:
 - a. WB_out gets the memory output in load case and in other cases gets the alu1 output.
 - b. This block checks if WB_out is zero
3. C_WB comes from the carry of the alu1

Control points:

1. Wr_en mux \Rightarrow 0
2. Rf_a3_mux \Rightarrow 1
3. Rf_a2_mux \Rightarrow 2
4. alu_out_mux \Rightarrow 3
5. Mem_out_mux \Rightarrow 4
6. MEM_WB_en \Rightarrow 5

Pipeline Register Contents

Pipeline Register	Components	Length(bits)
IFID	PC	16
	PCplus1	16
	instruction	16
IDRR	Alu opcode	1
	Op type(z/c)	2
	main_opcode	4
	Control points	6
	rf_a1	3
	rf_a2	3
	rf_a3	3
	pe_out	3
	sign extended values	16
	wr_en	1
	mem_wr_en	1
	carry_en	1
	zero_en	1
	pc	16
	pcplus1	16
RREX	Alu opcode	1
	Op type(z/c)	2
	main_opcode	4
	Control points	6
	Alu input 1	16
	Alu input 2	16
	Sign extended value/rf output	16
	PC	16
	mem_wr_en	1
	carry_en	1
	zero_en	1
EXMM	Op type(z/c)	2
	main_opcode	4
	Control points	6
	mem_wr_en	1

	zero_en	1
	Memory address	16
	Memory data in	16
	pc	16
MMWB	Main_opcode	4
	carry	1
	Control points	8
	Zero_en	1
	Mem output/mem address	16
	pc	16